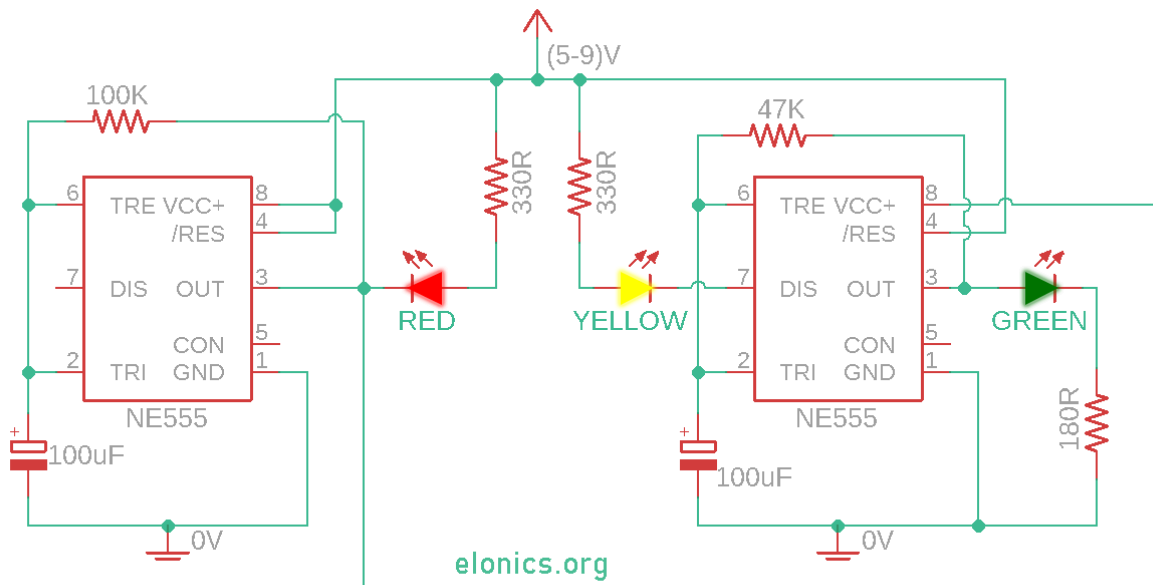


## Traffic Light Control system using 555 Timer IC

### COMPONENT :

- 2 x 555 Timer ICs
- LEDs: 1 Red, 1 Yellow, 1 Green
- Resistors: 100K, 47K, 2 x 330R, 180R
- Capacitors: 2 x 100uF
- Breadboard
- Few Breadboard Connectors
- (5-12)V Power Supply

### BLOCK / CIRCUIT DIAGRAM :



## MODEL TRAFFIC LIGHTS CIRCUIT

